

**K. J. SOMAIYA COLLEGE OF ENGINEERING**  
**DEPARTMENT OF ELECTRONICS ENGINEERING**  
**ELECTRONIC CIRCUITS**  
**Single Stage BJT Amplifier**

**Numerical 1:** For the circuit shown in figure 1, Determine  $I_{CQ}$ ,  $V_{CEQ}$  and  $A_V$

Given:  $\beta = 75$ ,  $r_o = \infty \Omega$

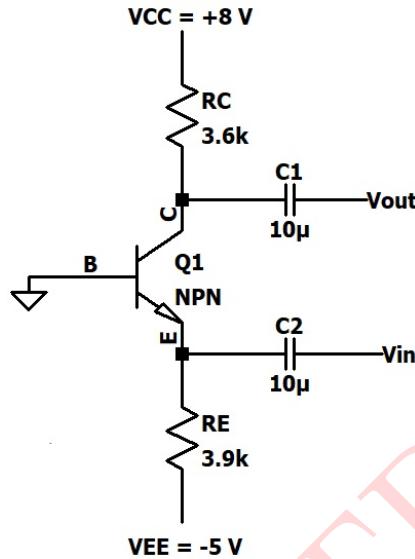


Figure 1: Circuit 1

**Solution:**

The given circuit 1 is a common base configuration employing npn BJT.

For DC biasing, the capacitors acts as an open source.

**DC Analysis:**

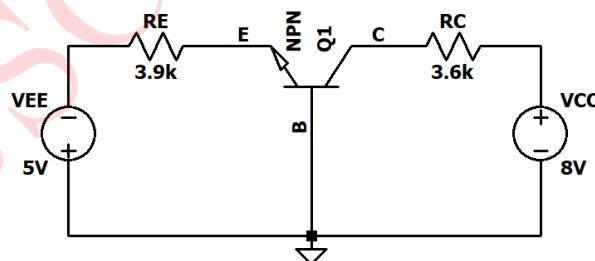


Figure 2: DC Biasing Circuit

$I_E$  can be calculated by applying KVL to the base-emitter loop,

$$-R_E I_E - V_{BE} + V_{EE} = 0$$

$$R_E I_E = V_{EE} - V_{BE}$$

$$I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

$$I_E = \frac{5 - 0.7}{3.9 \times 10^3} = 1.1 \text{ mA}$$

$$I_B = \frac{I_E}{1 + \beta} \quad \dots (\because I_E = (1 + \beta)I_B)$$

$$I_B = \frac{1.1 \times 10^{-3}}{1 + 75} = 14.5 \mu\text{A}$$

$$I_{CQ} = \beta I_B$$

$$I_{CQ} = 75 \times 14.47 \times 10^{-6} = 1.08 \mu\text{A}$$

$V_{CEQ}$  can be calculated by applying KVL to the collector-emitter loop,

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E + V_{EE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E + V_{EE}$$

$$V_{CE} = 8 - 1.08 \times 10^{-3} \times 3.6 \times 10^3 - 1.1 \times 10^{-3} \times 3.9 \times 10^3 + 5 = 4.822 \text{ V}$$

**AC Analysis:**

$$r_\pi = \frac{\beta V_T}{I_E}$$

$$r_\pi = \frac{75 \times 26 \times 10^{-3}}{1.1 \times 10^{-3}} = 1.77 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$g_m = \frac{1.08 \times 10^{-3}}{26 \times 10^{-3}} = 41.538 \text{ mA/V}$$

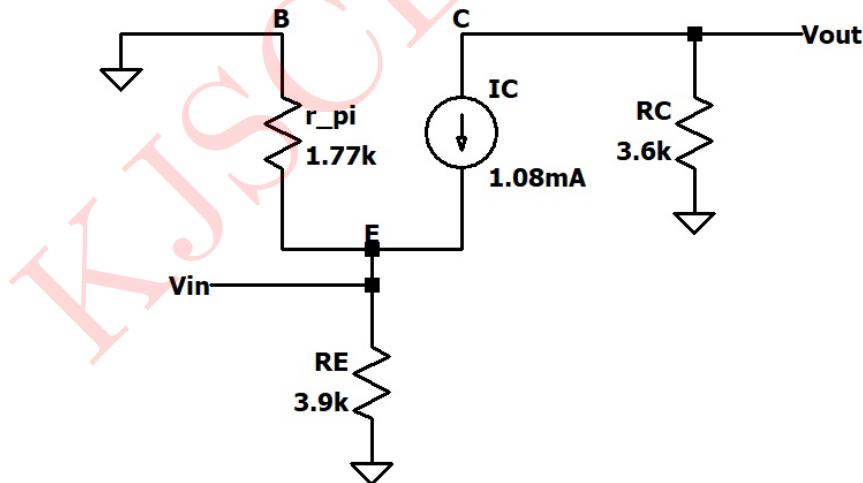


Figure 3: Small Signal Equivalent Circuit

**Input Impedance:**

$$R_i = \frac{r_\pi}{1 + \beta}$$

$$R_i = \frac{1.77 \times 10^3}{1 + 75} = 23.29 \Omega$$

**Output Impedance:**

$$R_o = R_C = 3.6 \text{ k}\Omega$$

**Voltage Gain:**

$$A_V = \frac{V_o}{V_i}$$

$$A_V = \frac{-g_m V_\pi R_C}{-V_\pi}$$

$$A_V = g_m R_C$$

$$A_V = 41.538 \times 10^{-3} \times 3.6 \times 10^3 = \mathbf{149.54}$$

### SIMULATED RESULT:

Above circuit is simulated in LTspice. The results are presented below:

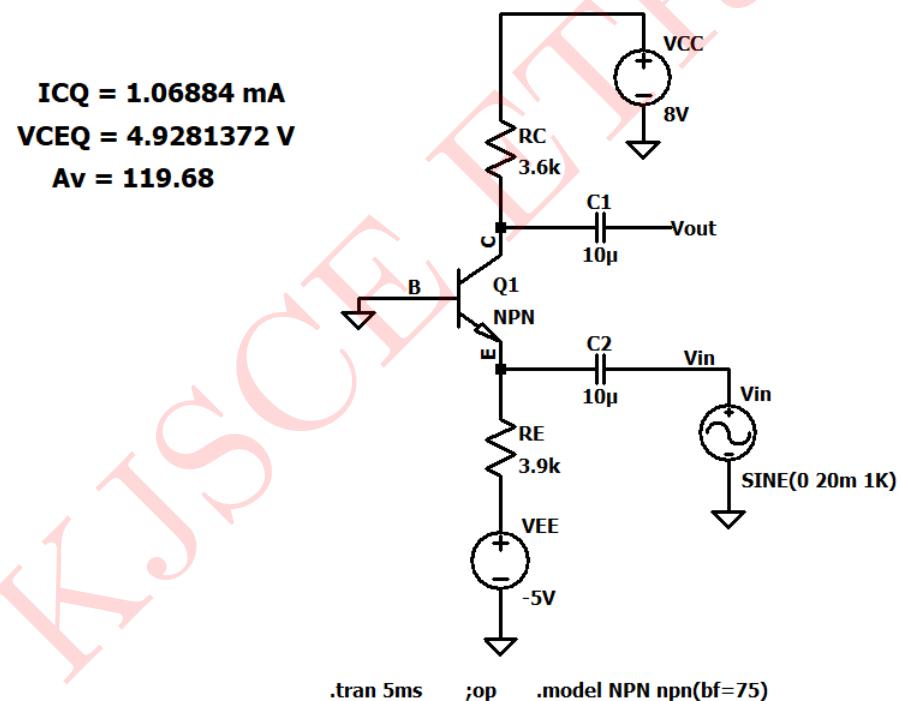


Figure 4: Circuit Schematic 1: Results

The input and output waveforms are shown in figure 5.

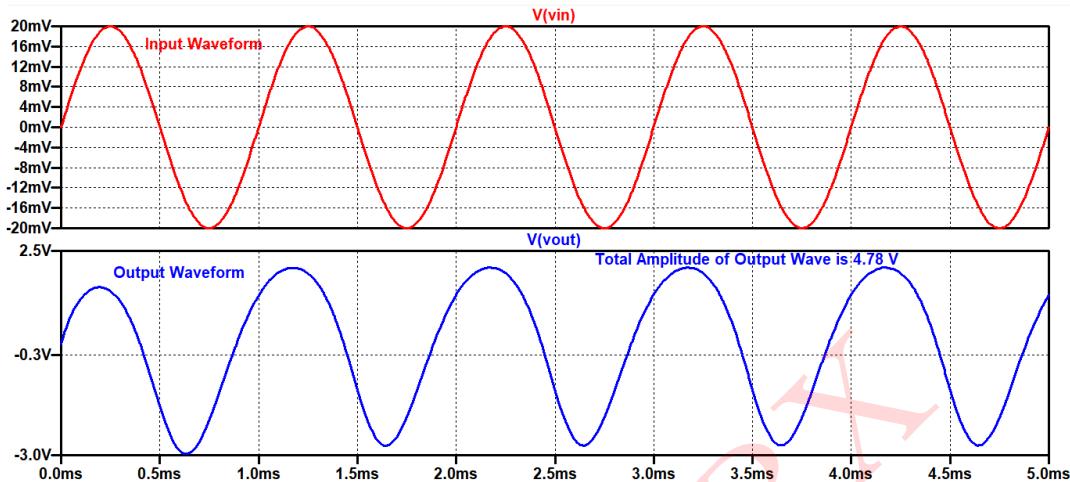


Figure 5: Input & Output waveforms

**Comparison of theoretical and simulated values:**

Parameters	Theoretical Values	Simulated Values
$I_{CQ}$	1.08 mA	1.0688 mA
$V_{CEQ}$	4.822 V	4.9281 V
$A_V$	149.54	119.68

Table 1: Numerical 1

**Numerical 2:** For the circuit shown in figure 6, Determine  $r_\pi$ ,  $Z_i$ ,  $Z_o$  and  $A_V$   
 Given:  $\beta = 120$ ,  $r_o = 40 \text{ k}\Omega$

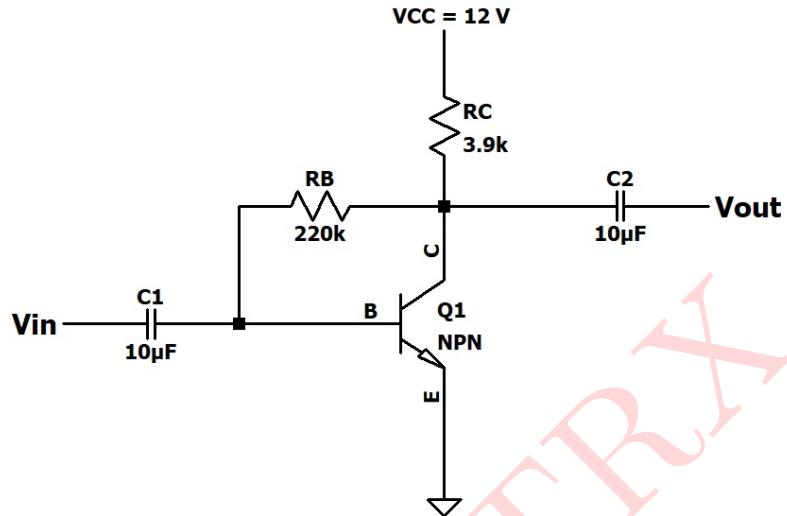


Figure 6: Circuit 2

**Solution:**

The given circuit 2 is a collector feedback configuration.

For DC biasing, the capacitors will act as an open source.

**DC Analysis:**

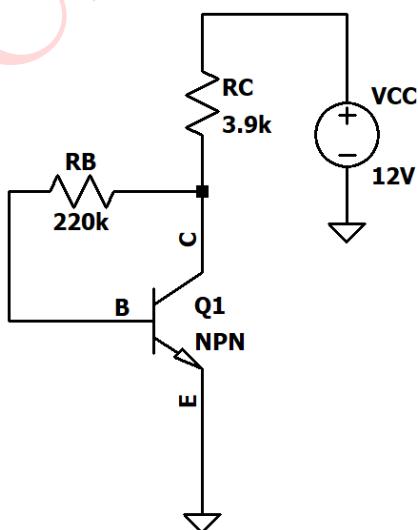


Figure 7: DC Biasing Circuit

$I_B$  can be calculated by applying KVL to the base-emitter loop,

$$V_{CC} - (I_C + I_B)R_C - I_B R_B - V_{BE} = 0$$

$$I_B R_B + (I_C + I_B)R_C = V_{CC} - V_{BE}$$

$$I_B R_B + (1 + \beta)I_B R_C = V_{CC} - V_{BE} \quad \dots (\because I_C = \beta I_B)$$

$$I_B(R_B + (1 + \beta)R_C) = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta)R_C}$$

$$I_B = \frac{12 - 0.7}{220 \times 10^3 + (1 + 120) \times 3.9 \times 10^3} = \mathbf{16.33 \mu A}$$

$$I_{CQ} = \beta I_B$$

$$I_{CQ} = 120 \times 16.33 \times 10^{-6} = \mathbf{1.96 mA}$$

$V_{CEQ}$  can be calculated by applying KVL to the collector-emitter loop,

$$V_{CC} - (I_C + I_B)R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - (I_C + I_B)R_C$$

$$V_{CE} = 12 - (1.96 \times 10^{-3} + 16.33 \times 10^{-6})3.9 \times 10^3 = \mathbf{4.29 V}$$

#### AC Analysis:

$$r_\pi = \frac{\beta V_T}{I_{CQ}}$$

$$r_\pi = \frac{120 \times 26 \times 10^{-3}}{1.96 \times 10^{-3}} = \mathbf{1.59 k\Omega}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$g_m = \frac{1.96 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{75.38 mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$V_A = r_o I_{CQ}$$

$$V_A = 40 \times 10^3 \times 1.96 \times 10^{-3} = \mathbf{78.4 V}$$

Small Signal Equivalent Circuit,

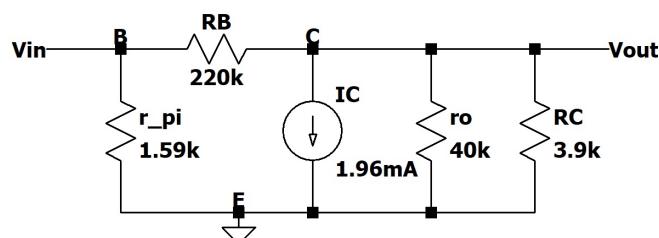


Figure 8: Small Signal Equivalent Circuit

Simplifying the above circuit with miller's theorem,

$$R_1 = \frac{R_B}{1 - A_V} \text{ and } R_2 = \frac{A_V}{A_V - 1} R_B$$

The voltage gain is much greater than 1.

$$\therefore R_2 \simeq R_B \quad \dots(1)$$

Small signal equivalent circuit after miller's theorem,

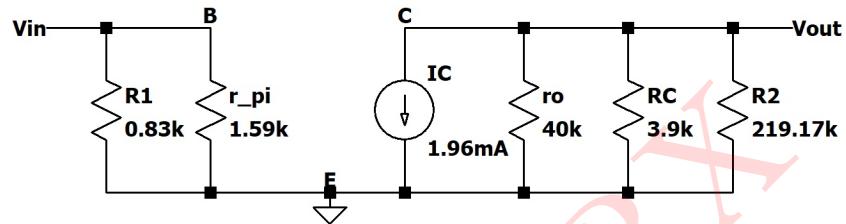


Figure 9: Small Signal Equivalent Circuit after Miller's Theorem

#### Voltage Gain:

$$A_V = \frac{V_o}{V_i}$$

$$A_V = \frac{-g_m V_\pi (r_o \parallel R_C \parallel R_2)}{V_\pi}$$

$$A_V = -g_m (r_o \parallel R_C \parallel R_2) \quad \dots(\text{from 1})$$

$$A_V = -75.38 \times 10^{-3} (40 \times 10^3 \parallel 3.9 \times 10^3 \parallel 220 \times 10^3)$$

$$A_V = -75.38 \times 10^{-3} \times 3.497 \times 10^3 = -263.6 \text{ V}$$

Negative sign indicates that input and output are out of phase.

$$R_1 = \frac{R_B}{1 - A_V}$$

$$R_1 = \frac{220 \times 10^3}{1 + 263.6} = 10.83 \text{ k}\Omega$$

$$R_2 = \frac{A_V}{A_V - 1} R_B$$

$$R_2 = \frac{-263.6}{-263.6 - 1} \times 220 \times 10^3 = 219.17 \text{ k}\Omega \simeq R_B$$

$$Z_i = R_1 \parallel r_\pi$$

$$Z_i = 0.83 \times 10^3 \parallel 1.59 \times 10^3 = 0.54 \text{ k}\Omega$$

$$Z_o = r_o \parallel R_C \parallel R_2$$

$$Z_o = 40 \times 10^3 \parallel 3.9 \times 10^3 \parallel 219.17 \times 10^3 = 3.496 \text{ k}\Omega$$

## SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

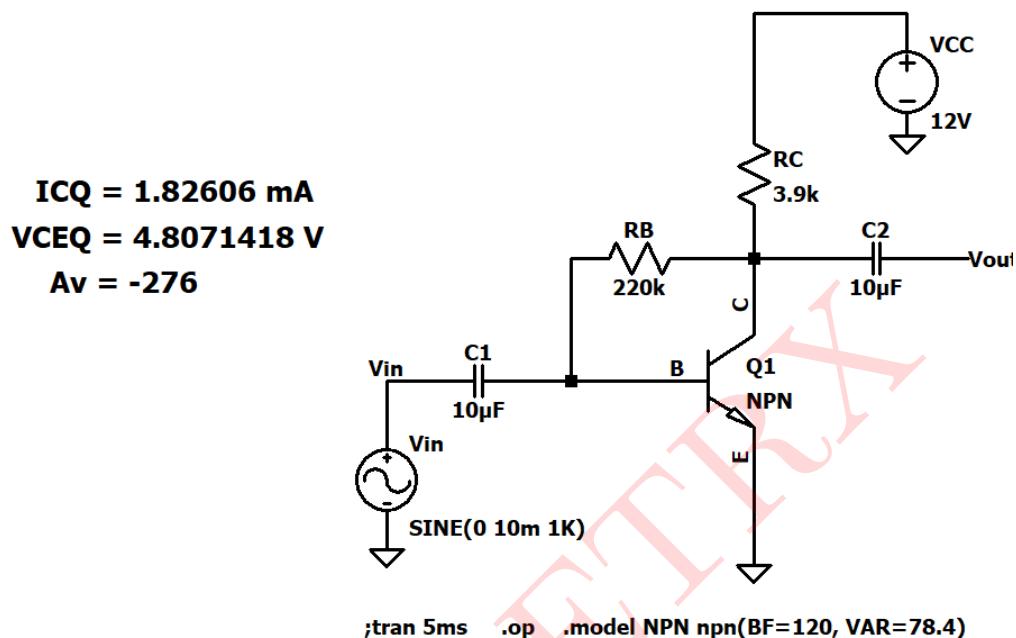


Figure 10: Circuit Schematic 2: Results

The input and output waveforms are shown in figure 11.

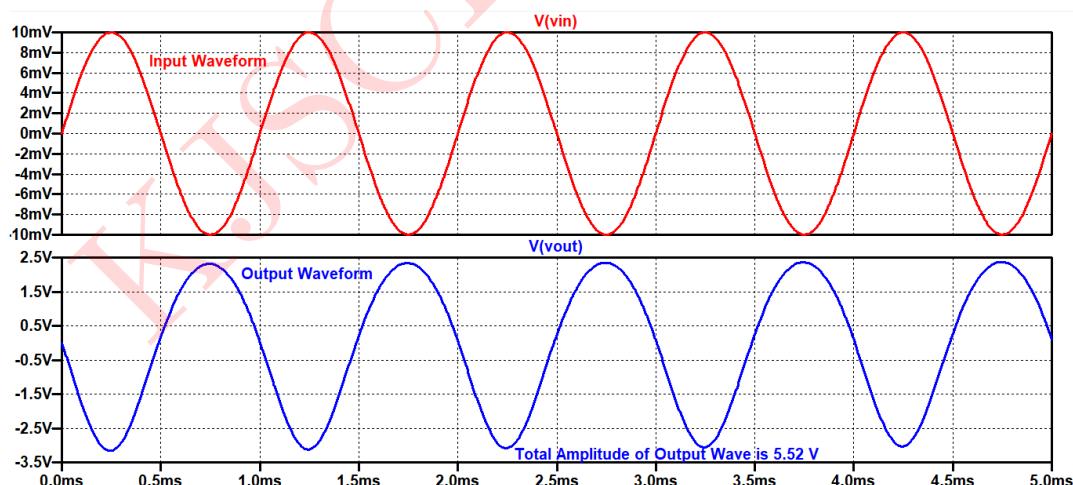


Figure 11: Input & Output waveforms

**Comparison of theoretical and simulated values:**

Parameters	Theoretical Values	Simulated Values
$I_{CQ}$	1.96 mA	1.826 mA
$V_{CEQ}$	4.29 V	4.8071 V
$A_V$	-263.6	-276

Table 2: Numerical 2

**Numerical 3:** The emitter follower has  $R_B = 74 \text{ k}\Omega$ ,  $R_E = 750 \Omega$ ,  $R_L = 5 \text{ k}\Omega$ ,  $R_S = 200 \Omega$ ,  $V_{CC} = 18 \text{ V}$  and  $V_{BE} = 0.7 \text{ V}$ . Assume  $\beta = 100$ ,  $V_A = 200 \text{ V}$ ,  $C_1 = C_2 = 10 \mu\text{F}$

- Find the Q-point defined by  $I_B$ ,  $I_C$  and  $V_{CE}$ .
- Calculate the small-signal parameters  $g_m$ ,  $r_\pi$  and  $r_o$  of the transistor.
- Calculate the input resistance  $R_{in} = V_S/i_S$ , the no-load voltage gain  $A_{VO} = V_o/V_b$ , the output resistance  $R_o$ , the overall voltage gain  $A_V = V_L/V_S$

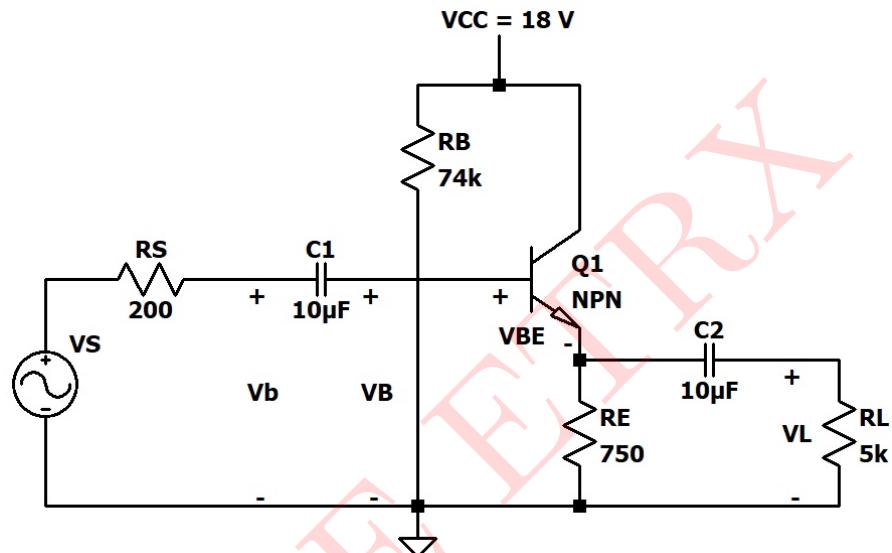


Figure 12: Circuit 3

#### Solution:

The given circuit 3 is an emitter-follower configuration.

For DC biasing, the capacitors will act as open sources.

#### DC Analysis:

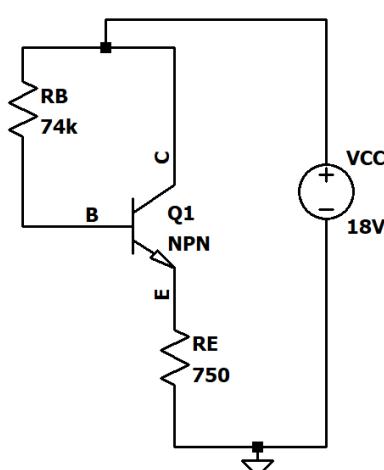


Figure 13: DC Biasing Circuit

a)  $I_{BQ}$  can be calculated by applying KVL to the base-emitter loop,

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_B R_B + (1 + \beta) I_B R_E = V_{CC} - V_{BE}$$

$\dots (\because I_E = (1 + \beta) I_B)$

$$I_B (R_B + (1 + \beta) R_E) = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1 + \beta) R_E}$$

$$I_B = \frac{18 - 0.7}{74 \times 10^3 + (1 + 100) \times 750} = \mathbf{115.52 \mu A}$$

$$I_{CQ} = \beta I_B$$

$$I_{CQ} = 100 \times 115.52 \times 10^{-6} = \mathbf{11.55 mA}$$

$$I_E = (1 + \beta) I_B$$

$$I_E = (1 + 100) \times 115.52 \times 10^{-6} = \mathbf{11.66 mA}$$

$V_{CEQ}$  can be calculated by applying KVL to the collector-emitter loop,

$$V_{CC} - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_E R_E$$

$$V_{CE} = 18 - 11.66 \times 10^{-3} \times 750 = \mathbf{9.255 V}$$

$$I_B = \mathbf{115.52 \mu A}, I_{CQ} = \mathbf{11.55 mA} \text{ & } V_{CEQ} = \mathbf{9.255 V}$$

#### AC Analysis:

$$\text{b) } g_m = \frac{I_{CQ}}{V_T}$$

$$g_m = \frac{11.55 \times 10^{-3}}{26 \times 10^{-3}} = \mathbf{444 mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}}$$

$$r_o = \frac{200}{11.55 \times 10^{-3}} = \mathbf{17.32 k\Omega}$$

$$r_\pi = \frac{\beta V_T}{I_E}$$

$$r_\pi = \frac{100 \times 26 \times 10^{-3}}{11.66 \times 10^{-3}} = \mathbf{222.98 \Omega}$$

$$g_m = \mathbf{444 mA/V}, r_o = \mathbf{17.32 k\Omega} \text{ and } r_\pi = \mathbf{222.98 \Omega}$$

c) Small Signal Equivalent Circuit,

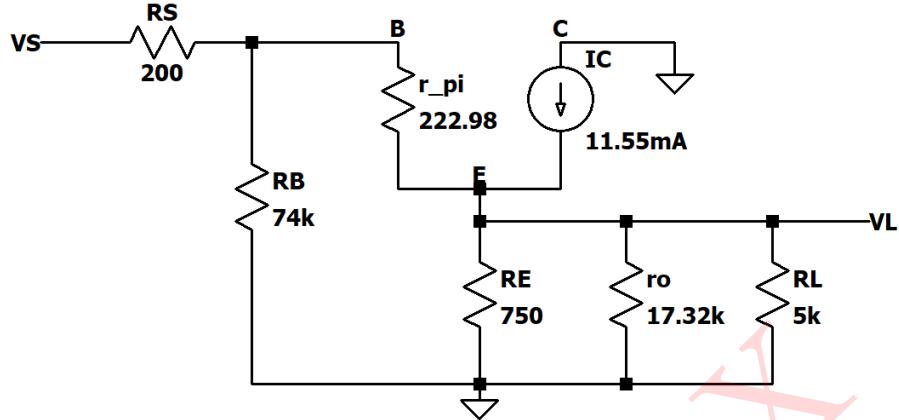


Figure 14: Small Signal Equivalent Circuit

Input Resistance:

Applying KVL to the input loop,

$$V_b = I_b r_\pi + (1 + \beta) I_b R_E$$

$$\frac{V_b}{I_b} = r_\pi + (1 + \beta) R_E$$

$$R' = r_\pi + (1 + \beta) R_E$$

We know,  $R_i = R_B \parallel R'$

$$R_i = R_B \parallel [r_\pi + (1 + \beta) R_E]$$

$$R_i = 74 \times 10^3 \parallel [222.98 + (1 + 100) \times 750]$$

$$R_i = 74 \times 10^3 \parallel 75.97 \times 10^3 = 37.48 \text{ k}\Omega$$

Output Resistance:

Let,  $V_S = 0$

$$\therefore R' = (R_S \parallel R_B) + r_\pi$$

$$R_o = \frac{R'}{(1 + \beta)} \parallel (r_o \parallel R_E)$$

$$R_o = \frac{(R_S \parallel R_B) + r_\pi}{(1 + \beta)} \parallel (r_o \parallel R_E)$$

$$R_o = \frac{(200 \parallel 74 \times 10^3) + 222.98}{1 + 100} \parallel (17.32 \times 10^3 \parallel 750)$$

$$R_o = 4.18 \parallel 718.87 = 4.15 \Omega$$

No-load voltage gain:

Output voltage  $V_o$  = voltage developed across  $(r_0 \parallel R_E)$

$$V_o = I_b(r_o \parallel R_E) + I_C(r_0 \parallel R_E)$$

$$V_o = I_b(r_o \parallel R_E) + \beta I_b(r_0 \parallel R_E)$$

$$V_o = (1 + \beta) I_b(r_0 \parallel R_E) \quad \dots(1)$$

$I_b$  can be written as,

$$I_b = \frac{V_\pi}{r_\pi}$$

$$I_b = \frac{V_b - V_e}{r_\pi}$$

but  $V_e = V_o$ ,

$$I_b = \frac{V_b - V_o}{r_\pi}$$

Substituting this in equation 1,

$$V_o = (1 + \beta) \left( \frac{V_b - V_o}{r_\pi} \right) (r_0 \parallel R_E)$$

$$V_o = \frac{(1 + \beta)V_b(r_0 \parallel R_E)}{r_\pi} - \frac{(1 + \beta)V_o(r_0 \parallel R_E)}{r_\pi}$$

$$V_o + \frac{(1 + \beta)V_o(r_0 \parallel R_E)}{r_\pi} = \frac{(1 + \beta)V_b(r_0 \parallel R_E)}{r_\pi}$$

$$V_o \left[ 1 + \frac{(1 + \beta)(r_0 \parallel R_E)}{r_\pi} \right] = \frac{(1 + \beta)V_b(r_0 \parallel R_E)}{r_\pi}$$

$$V_o \left[ \frac{r_\pi + (1 + \beta)(r_0 \parallel R_E)}{r_\pi} \right] = \frac{(1 + \beta)V_b(r_0 \parallel R_E)}{r_\pi}$$

$$\frac{V_o}{V_b} = \frac{(1 + \beta)(r_0 \parallel R_E)}{r_\pi} \times \frac{r_\pi}{r_\pi + (1 + \beta)(r_0 \parallel R_E)}$$

$$A_{VO} = \frac{(1 + \beta)(r_0 \parallel R_E)}{r_\pi + (1 + \beta)(r_0 \parallel R_E)}$$

$$A_{VO} = \frac{(1 + 100)(17.32 \times 10^3 \parallel 750)}{222.98 + (1 + 100)(17.32 \times 10^3 \parallel 750)}$$

$$A_{VO} = \frac{(101)(718.87)}{222.98 + (101)(718.87)} = \mathbf{0.9969}$$

Overall Voltage Gain:

Output voltage  $V_o$  = voltage developed across  $(r_o \parallel R_E \parallel R_L)$

$$V_L = I_e(r_o \parallel R_E \parallel R_L)$$

$$V_L = (1 + \beta)I_b(r_o \parallel R_E \parallel R_L)$$

...(2)

$I_b$  can be written as,

$$I_b = \frac{V_\pi}{r_\pi} = \frac{V_b - V_e}{r_\pi}$$

but  $V_e = V_L$ ,

$$I_b = \frac{V_b - V_L}{r_\pi}$$

Substituting this in equation 2,

$$V_L = (1 + \beta) \left( \frac{V_b - V_L}{r_\pi} \right) (r_o \parallel R_E \parallel R_L)$$

$$V_L = \frac{(1 + \beta)V_b}{r_\pi} (r_o \parallel R_E \parallel R_L) - \frac{(1 + \beta)V_L}{r_\pi} (r_o \parallel R_E \parallel R_L)$$

$$V_L \left[ 1 + \frac{(1 + \beta)}{r_\pi} (r_o \parallel R_E \parallel R_L) \right] = \frac{(1 + \beta)V_b}{r_\pi} (r_o \parallel R_E \parallel R_L)$$

$$V_L [r_\pi + (1 + \beta)(r_o \parallel R_E \parallel R_L)] = (1 + \beta)V_b(r_o \parallel R_E \parallel R_L) \quad \dots(3)$$

but by voltage divider we get,

$$V_b = \left( \frac{R_i}{R_i + R_S} \right) V_S$$

Where,  $R_i = R_B \parallel [r_\pi + (1 + \beta)R_E]$

Substituting  $V_b$  in equation 3,

$$V_L [r_\pi + (1 + \beta)(r_o \parallel R_E \parallel R_L)] = (1 + \beta)(r_o \parallel R_E \parallel R_L) \left( \frac{R_i}{R_i + R_S} \right) V_S$$

$$\frac{V_L}{V_S} = \frac{(1 + \beta)(r_o \parallel R_E \parallel R_L)}{r_\pi + (1 + \beta)(r_o \parallel R_E \parallel R_L)} \times \left( \frac{R_i}{R_i + R_S} \right)$$

$$A_V = \frac{(1 + 100)(17.32 \times 10^3 \parallel 750 \parallel 5 \times 10^3)}{222.98 + (1 + 100)(17.32 \times 10^3 \parallel 750 \parallel 5 \times 10^3)} \times \left( \frac{37.48 \times 10^3}{37.48 \times 10^3 + 200} \right)$$

$$A_V = \frac{(101)(628.5)}{222.98 + (101)(628.5)} \times 0.9945 = 0.991$$

$R_i = 37.48 \text{ k}\Omega$ ,  $R_o = 4.15 \Omega$ ,  $A_{VO} = 0.9969$  &  $A_V = 0.991$

### SIMULATED RESULTS:

Above circuit is simulated in LTspice. The results are presented below:

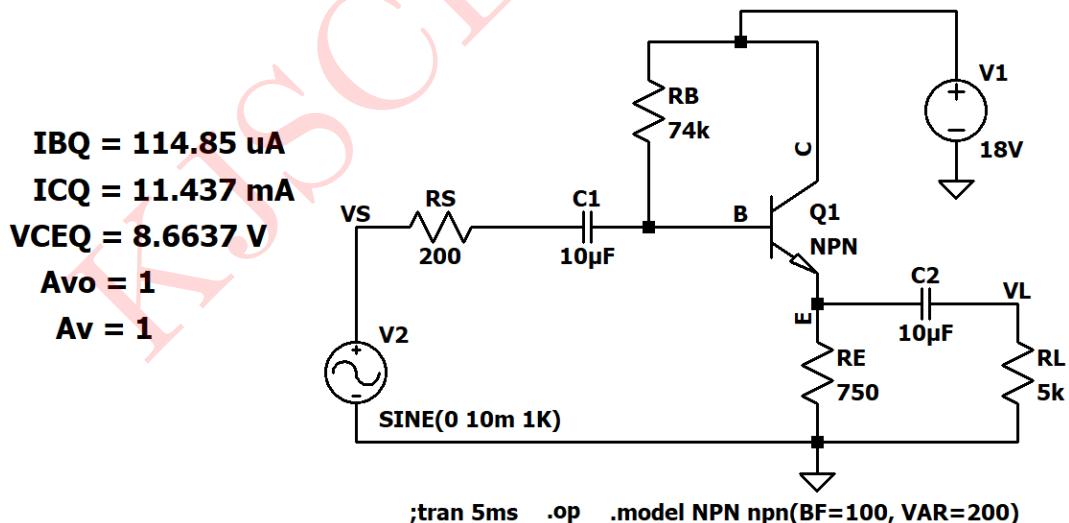


Figure 15: Circuit Schematic 3: Results

The input and output waveforms are shown in figure 16.

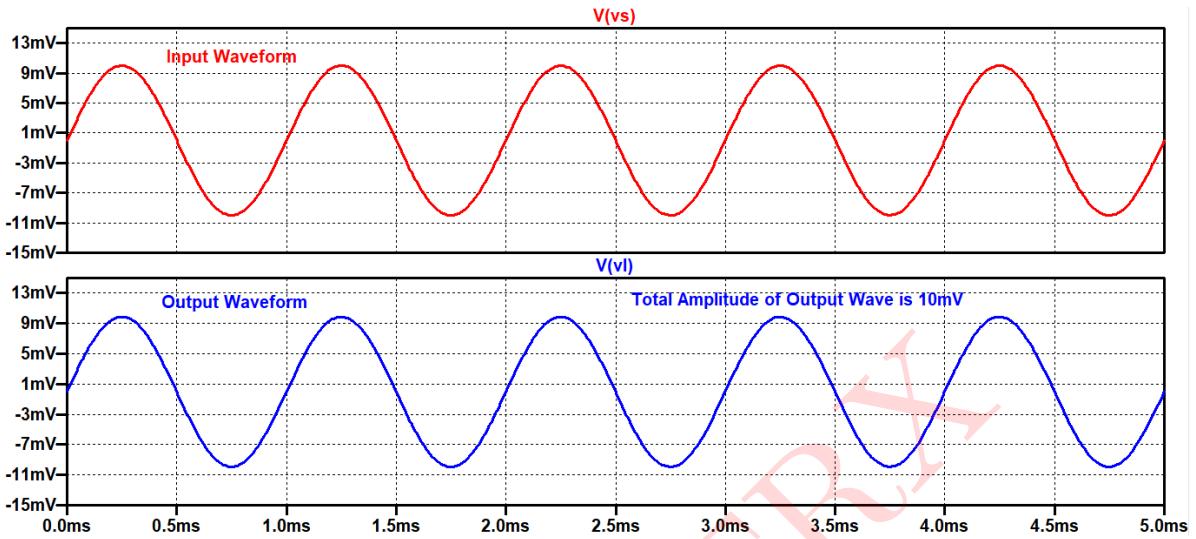


Figure 16: Input & Output waveforms

#### Comparison of theoretical and simulated values:

Parameters	Theoretical Values	Simulated Values
$I_{BQ}$	$115.52 \mu\text{A}$	$114.85 \mu\text{A}$
$I_{CQ}$	$11.55 \text{ mA}$	$11.437 \text{ mA}$
$V_{CEQ}$	$9.255 \text{ V}$	$8.6637 \text{ V}$
$A_{VO}$	$0.9969$	$1$
$A_V$	$0.991$	$1$

Table 3: Numerical 3

\*\*\*\*\*